

Complete each wire by connecting it to the panel. If a wire is named a color, use that color to complete the wire. If it does not name a color use your pencil to draw the wire.

- SEF
- Pink
- DP
- EFP4
- Brown
- E1
- Orange
- LC
- Gray
- Purple

○ TV-1		TV-10 ○
○ TV-2		TV-11 ○
○ TV-3		TV-12 ○
○ TV-4		CVT ○
○ TV-5		FTI ○
○ TV-6		EFP3 ○
○ TV-7		EFP4 ○
○ TV-8		DOW-1 ○
○ TV-9		DOW-2 ○

- A2
- Yellow
- IDM
- Red
- ICT
- +4v
- EFP3
- Green
- A1
- Blue



As a final touch, the mechanic must make sure he tightens a screw besides each location. This prevents the wires from falling out.

Would you like to be a mechanic and connect the wires to the panel box? Why or why not?

---



---



---